



RAN - 1803000201030092



**RAN-1803000201030092**

**F. Y. B. Sc. Electronics (Sem. - I) Examination**

**March - 2023**

**Electronics : Paper - II**

**Digital Electronics Circuits**

**[ Total Marks: 50**

**સૂચના : / Instructions**

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.  
**Fill up strictly the details of signs on your answer book**

Name of the Examination:

**F. Y. B. Sc. Electronics (Sem. - I)**

Name of the Subject :

**Electronics : Paper - II Digital Electronics Circuits**

Subject Code No.: **1803000201030092**

Seat No.:

<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>
----------------------	----------------------	----------------------	----------------------	----------------------	----------------------

Student's Signature

- (2) Figure on the right indicates full marks
- (3) All symbols and abbreviations have their usual meaning.
- (4) Non-programmable calculators are allowed.
- (5) Assume data if necessary.

***O.M.R. Sheet ભરવા અંગેની અગત્યની સૂચનાઓ આપેલ  
O.M.R. Sheetની પાછળ છાપેલ છે.***

***Important instructions to fillup O.M.R. Sheet  
are given on back side of the provided O.M.R. Sheet.***

- Q. 1.** An AND gate
- A. Implements logic addition
  - B. Is equivalent to a series switching circuit
  - C. Is an any-or-all gate
  - D. Is equivalent to a parallel switching circuit
- Q. 2.** Which of the following is not an octal number?
- A. 14
  - B. 28
  - C. 210
  - D. 77
- Q. 3.** What is the major difference between half-adders and full-adders?
- A. Nothing basically; full-adders are made up of two half-adders.
  - B. Full adders can handle double-digit numbers.
  - C. Full adders have a carry input capability.
  - D. Half adders can handle only single-digit numbers.
- Q. 4.** The range of voltages between  $V_{L(max)}$  and  $V_{H(min)}$  are \_\_\_\_\_.
- A. Unknown
  - B. Unnecessary
  - C. Unacceptable
  - D. None of the above
- Q. 5.** The binary addition  $1 + 1 + 1$  gives
- A. 111
  - B. 11
  - C. 110
  - D. 3
- Q. 6.** An XOR gate produces an output high only when its two inputs are
- A. High
  - B. Low
  - C. Different
  - D. Same
- Q. 7.** A positive AND gate is also a negative
- A. NAND gate
  - B. NOR gate
  - C. AND gate
  - D. OR gate

- Q. 8.** A unique advantageous features of CMOS family is its
- A. Use of NMOS circuits
  - B. Power dissipation in nanowatt range
  - C. Speed
  - D. Dependence on frequency for power dissipation
- Q. 9.** The code in which if successive code is one binary number more than its preceding code called the \_\_\_\_\_.
- A. Reflective code
  - B. Sequential code
  - C. Gray code
  - D. EBCDIC code
- Q. 10.** The 1's complement of 10110011 is \_\_\_\_\_.
- A. 01100001
  - B. 10011001
  - C. 01011101
  - D. 01001100
- Q. 11.** The hexadecimal digits are 0 to 9 and \_\_\_\_\_.
- A. A to E
  - B. A to F
  - C. A to G
  - D. A to Z
- Q. 12.** The output of an AND gate is LOW \_\_\_\_\_.
- A. All the time
  - B. When any input is LOW
  - C. When any input is HIGH
  - D. When all inputs are HIGH
- Q. 13.** What are the two types of basic adder circuits?
- A. Sum and carry
  - B. Half-adder and full-adder
  - C. Asynchronous and synchronous
  - D. One and two's complement

- Q. 14.** The ASCII
- A. Is a subset of 8-bit EBCDIC
  - B. Is used only in Western Countries
  - C. Is version II of the ASC Standard
  - D. Has 128 characters, including 32 control characters
- Q. 15.** How many basic binary subtraction operations are possible?
- A. 4
  - B. 3
  - C. 2
  - D. 1
- Q. 16.** Which of the following combinations cannot be combined into K-map groups?
- A. Corners in the same column
  - B. Corners in the same row
  - C. Overlapping combinations
  - D. Diagonal corners
- Q. 17.** The active switching element used in all TTL circuits is the \_\_\_\_\_.
- A. BJT
  - B. FET
  - C. UJT
  - D. MOSFET
- Q. 18.** Which of the following is an invalid BCD code?
- A. 0011
  - B. 1100
  - C. 1000
  - D. 0001
- Q. 19.** The binary addition  $1 + 1 + 1$  gives
- A. 111
  - B. 11
  - C. 110
  - D. 3
- Q. 20.** A multiplexer has \_\_\_\_\_.
- A. One input and several outputs
  - B. One input and one output
  - C. Several inputs and several outputs
  - D. Several inputs and one output

- Q. 21. Which of the following expressions is in the sum-of-products (SOP) form?
- A.  $(A + B)(C + D)$                       B.  $(A)B(CD)$   
C.  $AB(CD)$                                 D.  $AB + CD$
- Q. 22. The difference of  $BC_5 - A_2B$  equals \_\_\_\_\_.
- A.  $A_{19}$                                         B.  $A_{2B}$   
C.  $19A$                                         D.  $198$
- Q. 23. The binary numbers  $A = 1100$  and  $B = 1001$  are applied to the inputs of a comparator. What are the output levels?
- A.  $A > B = 1, A < B = 0, A = B = 1$   
B.  $A > B = 0, A < B = 1, A = B = 0$   
C.  $A > B = 1, A < B = 0, A = B = 0$   
D.  $A > B = 0, A < B = 1, A = B = 1$
- Q. 24. Convert the fractional decimal number 6.75 to binary.
- A.  $0111.1100$                                 B.  $0110.1010$   
C.  $0110.1100$                                 D.  $0110.0110$
- Q. 25. A full-adder has a  $C_{in} = 0$ . What are the sum ( $\Sigma$ ) and the carry ( $C_{out}$ ) when  $A = 1$  and  $B = 1$ ?
- A.  $\Sigma = 0, C_{out} = 0$                       B.  $\Sigma = 0, C_{out} = 1$   
C.  $\Sigma = 1, C_{out} = 0$                       D.  $\Sigma = 1, C_{out} = 1$
- Q. 26. The sum of  $11011 + 10111$  equals \_\_\_\_\_.
- A.  $110010$                                     B.  $100001$   
C.  $110100$                                     D.  $100100$



**Q. 34.** How many binary bits are necessary to represent 100 decimal numbers?

A. 9

B. 7

C. 10

D. 8

**Q. 35.** Convert  $173_8$  to decimal.

A. 216

B. 173

C. 3D9

D. 123

\_\_\_\_\_

**SPACE FOR ROUGH WORK**