



R A N - 1 9 0 3 0 0 0 2 0 2 0 3 0 0 9 1

RAN-1903000202030091**F.Y.B.Sc. (Sem. II) Examination April - 2023****Electronics : Paper I - Semiconductor Devices****[Total Marks: 50****सूचना : / Instructions**

(१)

नीचे दशविले निशानीवाणी विगतो उत्तरवली पर अवश्य लपववी.
Fill up strictly the details of signs on your answer book

Name of the Examination:

F.Y.B.Sc. (Sem. II)

Name of the Subject :

Electronics : Paper I - Semiconductor Devices

Subject Code No.: 1903000202030091

Seat No.:

Student's Signature

- (2) Figure on the right indicates full marks
- (3) All symbols and abbreviations have their usual meaning.
- (4) Non-programmable calculators are allowed.
- (5) Assume data if necessary.

Q-1 Answer in short:**08**

- (a) Why collector is made larger than emitter and base?
- (b) Define: frequency
- (c) What is full form of LED and LCD?
- (d) Draw the symbol of (i) FET (ii) UJT

Q-2 (a) Discuss the construction and working of Clamper circuit.**10**

- (b) Draw the sin wave and show the peak voltage, peak-peak voltage, time period.

04**OR****Q-2 (a) What is transistor? Discuss the constructional details of a transistor.****10**

- (b) Derive: $1 - \alpha = 1 / (1 + \beta)$

04

- Q-3** (a) Explain the construction and working of a UJT. **10**
(b) The intrinsic stand-off ratio for a silicon UJT is determined to be 0.6 and $V_{BB} = 12V$. Find the value of V_A and V_P ? **04**

OR

- Q-3** (a) Give full form of LED. Discuss the construction and working of LED. **10**
(b) Give some applications of LED. **04**

- Q-4 Write short note on (Any TWO)** **14**
(a) Clipper circuits
(b) N-channel JFET
(c) Load line
(d) Depletion mode MOSFET
-