



RAN - 1903000203020093



RAN-1903000203020093

S. Y. B. Sc. (Electronics) (Sem. - III) Examination

March - 2023

Electronics : Paper - V

Linear Power Electronics

સૂચના : / Instructions

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.
Fill up strictly the details of signs on your answer book

Name of the Examination:

S. Y. B. Sc. (Electronics) (Sem. - III)

Name of the Subject :

Electronics : Paper - V Linear Power Electronics

Subject Code No.: **1903000203020093**

Seat No.:

<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>
----------------------	----------------------	----------------------	----------------------	----------------------	----------------------

Student's Signature

(2) All questions are compulsory.

***O.M.R. Sheet ભરવા અંગેની અગત્યની સૂચનાઓ આપેલ
O.M.R. Sheetની પાછળ છાપેલ છે.
Important instructions to fillup O.M.R. Sheet
are given on back side of the provided O.M.R. Sheet.***

- Q. 7.** What type of regulators offer inherent short-circuits protection?
- A) Shunt regulators B) Series regulators
C) Three-terminal regulators D) Switching regulators
- Q. 8.** Voltage regulators keep a constant _____ output voltage when the input or load varies within limits.
- A) DC B) AC
C) Ripple D) None
- Q. 9.** Switching regulators are series type regulators, which has _____ power dissipation and _____ efficiency.
- A) Increased, increased B) Increased, reduced
C) Reduced, reduced D) Reduced, increased
- Q. 10.** The output voltage of a regulated power supply is affected by which of the following factors
- A) Input voltage B) Load current
C) Temperature D) All the above
- Q. 11.** A fixed voltage regulator can be a _____.
- A) Positive voltage regulator
B) Negative voltage regulator
C) Positive or negative voltage regulator
D) None of the above
- Q. 12.** A diode for which you can change the reverse bias, and thus vary the capacitance is called
- A) Varactor diode B) Tunnel diode
C) Zener diode D) Switching diode

- Q. 19.** In a Zener voltage regulator, the changes in load current produce changes in
- A) Zener current
 - B) Zener voltage
 - C) Zener voltage as well as Zener current
 - D) None of the above
- Q. 20.** A Zener voltage regulator will cease to act as a voltage regulator if Zener current becomes
- A) Less than load current
 - B) Zero
 - C) More than load current
 - D) None of the above
- Q. 21.** A Zener regulator _____ in the power supply.
- A) Increases the ripple
 - B) Decreases the ripple
 - C) Neither increases nor decreases the ripple
 - D) Data insufficient
- Q. 22.** Thermal shutdown occurs in an IC regulator if
- A) Power dissipation is too high
 - B) Internal temperature is too high
 - C) Current through the device is too high
 - D) None
- Q. 23.** Testing a good diode with an ohmmeter should indicate
- A) High resistance when forward or reverse biased
 - B) Low resistance when forward or reverse biased
 - C) High resistance when reverse biased and low resistance when forward biased
 - D) High resistance when forward biased and low resistance when reverse biased

- Q. 24.** The 79XX series of voltage regulators produces an output voltage that is
- A) Negative
 - B) Positive
 - C) Either Positive or negative
 - D) Unregulated
- Q. 25.** A shunt regulator is inefficient because
- A) It wastes power
 - B) It uses a series resistor and a shunt transistor
 - C) The ratio of output to input power is low
 - D) All of the above
- Q. 26.** A series regulator is more efficient than a shunt regulator because
- A) It has a series resistor
 - B) It can boost the voltage
 - C) The pass transistor replaces the series resistor
 - D) It switches the pass transistor on and off
- Q. 27.** Why is heat produced in a diode?
- A) Due to current passing through the diode
 - B) Due to voltage across the diode
 - C) Due to the power rating of the diode
 - D) Due to the PN junction of the diode
- Q. 28.** Which of the following circuits would require the least amount of filtering?
- A) A half-wave rectifier
 - B) A full-wave rectifier
 - C) A bridge rectifier
 - D) A full-wave rectifier and a bridge rectifier

SPACE FOR ROUGH WORK