



RAN - 1903000203020093



**RAN-1903000203020093**

**S. Y. B. Sc. (Electronics) (Sem. - III) Examination**

**March - 2023**

**Electronics : Paper - V**

**Linear Power Electronics**

**સૂચના : / Instructions**

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.  
**Fill up strictly the details of signs on your answer book**

Name of the Examination:

**S. Y. B. Sc. (Electronics) (Sem. - III)**

Name of the Subject :

**Electronics : Paper - V Linear Power Electronics**

Subject Code No.: **1903000203020093**

Seat No.:

<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>
----------------------	----------------------	----------------------	----------------------	----------------------	----------------------

Student's Signature

(2) All questions are compulsory.

***O.M.R. Sheet ભરવા અંગેની અગત્યની સૂચનાઓ આપેલ  
O.M.R. Sheetની પાછળ છાપેલ છે.***

***Important instructions to fillup O.M.R. Sheet  
are given on back side of the provided O.M.R. Sheet.***







- Q. 20.** The chemical energy in a battery or cell
- A) Is a form of kinetic energy
  - B) Cannot be replenished once it is gone
  - C) Changes to kinetic energy when the cell is used
  - D) Is caused by electric current
- Q. 21.** In a power supply diagram, which block indicates a pulsating dc output?
- A) Transformer
  - B) Filter
  - C) Rectifier
  - D) Regulator
- Q. 22.** The average value of the half-wave rectified output voltage is approximately \_\_\_\_\_ of  $V_p$
- A) 31.8%
  - B) 63.6%
  - C) 70.7%
  - D) 100%
- Q. 23.** A Zener diode is used as a \_\_\_\_\_ voltage regulating device.
- A) Shunt
  - B) Series
  - C) Series-shunt
  - D) None of the above
- Q. 24.** Another name for Zener diode is \_\_\_\_\_ diode.
- A) Breakdown
  - B) Voltage
  - C) Power
  - D) Current
- Q. 25.** In a Zener voltage regulator, the changes in load current produce changes in
- A) Zener current
  - B) Zener voltage
  - C) Zener voltage as well as Zener current
  - D) None of the above

- Q. 26.** A Zener voltage regulator will cease to act as a voltage regulator if Zener current becomes
- A) Less than load current
  - B) Zero
  - C) More than load current
  - D) None of the above
- Q. 27.** A Zener regulator \_\_\_\_\_ in the power supply.
- A) Increases the ripple
  - B) Decreases the ripple
  - C) Neither increases nor decreases the ripple
  - D) Data insufficient
- Q. 28.** Thermal shutdown occurs in an IC regulator if
- A) Power dissipation is too high
  - B) Internal temperature is too high
  - C) Current through the device is too high
  - D) None
- Q. 29.** Testing a good diode with an ohmmeter should indicate
- A) High resistance when forward or reverse biased
  - B) Low resistance when forward or reverse biased
  - C) High resistance when reverse biased and low resistance when forward biased
  - D) High resistance when forward biased and low resistance when reverse biased
- Q. 30.** The 79XX series of voltage regulators produces an output voltage that is
- A) Negative
  - B) Positive
  - C) Either Positive or negative
  - D) Unregulated
- Q. 31.** A shunt regulator is inefficient because
- A) It wastes power
  - B) It uses a series resistor and a shunt transistor
  - C) The ratio of output to input power is low
  - D) All of the above

**Q. 32.** A series regulator is more efficient than a shunt regulator because

- A) It has a series resistor
- B) It can boost the voltage
- C) The pass transistor replaces the series resistor
- D) It switches the pass transistor on and off

**Q. 33.** Why is heat produced in a diode?

- A) Due to current passing through the diode
  - B) Due to voltage across the diode
  - C) Due to the power rating of the diode
  - D) Due to the PN junction of the diode
-

**SPACE FOR ROUGH WORK**