



R A N - 2 0 0 3 0 0 0 2 0 4 0 2 0 0 9 1

**RAN-2003000204020091****S.Y.B.Sc. (Sem. IV) Examination April - 2023****Electronics (Paper III)****Amplifiers and Linear Integrated Circuits****सूचना : / Instructions**

(१)

नीचे दशविले निशानीवाणी विगतो उत्तरवही पर अवश्य लभवी.  
Fill up strictly the details of signs on your answer book

Name of the Examination:

S.Y.B.Sc. (Sem. IV)

Name of the Subject :

Electronics (Paper III )  
Amplifiers and Linear Integrated Circuits

Subject Code No.: 2003000204020091

Seat No.:

Student's Signature

- (2) Q.1 is compulsory.  
(3) Figures at extreme right indicate full marks.  
(4) Draw figures/diagrams to support your answer.  
(5) Assume data, if required.

**Q.1 Answer Briefly****8**

- a) Briefly explain feedback and the types of feedback.  
b) Give Barkhausen's criterion for oscillation  
c) Draw the circuit of Astable Multivibrator?  
d) What is the limitation of Class B push pull amplifier.

**Q.2** a) What is the effect of negative feedback on input and output impedance of voltage shunt amplifier?**8**

- b) A voltage series feedback amplifier has the following data: gain = 500,  $R_i = 1.5k\Omega$ ,  $R_o = 50k\Omega$ ,  $\beta = 1/20$ . Calculate the amplifier gain, input and output resistance with feedback

**6****OR**

- a) Explain the working principle of Bistable Multivibrator with neat diagram **8**  
b) To design an astable multivibrator of 1 khz having resistor of  $10k\Omega$ . **6**

- Q.3** a) Show that the power efficiency of a resistive load Class A power amplifier is 25% only what steps are taken to improve the power efficiency of Class A power amplifier **8**
- b) For a class A power amplifier, zero signal collector current is 80mA and  $V_{cc} = 10V$ . Calculate maximum ac power, dc power and maximum power efficiency. **6**

**OR**

- a) Explain circuit and working of Astable multivibrator. Draw the waveforms of the Astable multivibrator **8**
- b) Prove that the even harmonics are cancelled in push-pull amplifier **6**

**Q.4** Write short note on (any two). **14**

- a) Advantages of negative feedback
- b) Wein bridge oscillator
- c) Monostable multivibrator
- d) Fundamentals about tuned amplifier
-