



R A N - 2 1 0 3 0 0 0 2 0 6 0 2 0 0 9 1

**RAN-2103000206020091****T.Y.B.Sc. (Sem. VI) Examination April - 2023****Electronics : Paper VI - Linear Integrated Systems****Time: 2 Hours ]****[ Total Marks: 50****सूचना : / Instructions**

(१)

नीचे दशाविवेक निशानीवाणी विगतो उत्तरवली पर अवश्य लपववी.  
**Fill up strictly the details of signs on your answer book**

Name of the Examination:

☛ **T.Y.B.Sc. (Sem. VI)**

Name of the Subject :

☛ **Electronics : Paper VI - Linear Integrated Systems**Subject Code No.: **2103000206020091**

Seat No.:

Student's Signature

- (2) Figure on the right indicates full marks.
- (3) All symbols and abbreviations have their usual meaning.
- (4) Non-programmable calculators are allowed.
- (5) Q.1 is compulsory.
- (6) Assume data if necessary.

**Q:1****Answer in brief:****08**

1. Define the frequency response of an op-amp
2. What is Chebyshev response?
3. Explain half wave rectifier circuit using op-amp.
4. What causes the gain of the op-amp to roll off after a certain frequency is reached?

**Q:2**

- (A) Prove that the open loop voltage gain of the op- amp is a complex quantity and is a function of operating frequency.
- (B) An inverting amplifier using 741C must have a flat response up to 40 kHz. The gain of the amplifier is 20. What maximum peak to peak input signal can be applied without distorting the output?

**07****07****OR**

- Q:2** (A) Discuss in detail first order Butter worth low pass filter and its design principles. **08**
- (B) Design Second order Butterworth high pass filter using op-amp for a cut off frequency of 2 kHz. **06**
- Q:3** (A) Explain the working of successive-approximation ADC with neat diagram and an example. **07**
- (B) Explain all pass filter and its applications **07**
- OR**
- Q:3** (A) State Bark hausen criteria for oscillation. Discuss phase shift oscillator (IC 741) with necessary diagram, expressions and design principles. **08**
- (B) Explain different comparator circuit using op-amp. **06**
- Q:4** (A) Explain the working and design principles of free running multivibrator using IC741 **08**
- (B) Design a square wave oscillator so that  $f_0 = 3$  kHz. The op-amp is 741C with dc supply voltages =  $\pm 12$ v. **06**
- OR**
- Q:4** (A) Using the internal structure of IC 555, explain its action as an astable multivibrator. **07**
- (B) Design an astable multi vibrator using IC555 having an output frequency of 2 kHz with a duty cycle of 60%. **07**
-