



RAN - 2103000206021005

RAN-2103000206021005**B. Sc. (Sem. - VI) Examination April - 2023****Physics : Paper - X PH-610 (New)****Analog and Digital Electronics****[Total Marks: 50****સૂચના : / Instructions**

(1)

નીચે દર્શાવેલ નિશાનીવાળી વિગતો ઉત્તરવહી પર અવશ્ય લખવી.
Fill up strictly the details of signs on your answer book

Name of the Examination:

☛ **B. Sc. (Sem. - VI)**

Name of the Subject :

☛ **Physics : Paper - X PH-610 (New) Analog and Digital Electronics**Subject Code No.: **2103000206021005**

Seat No.:

Student's Signature

- (2) Draw neat diagrams wherever necessary.
- (3) Symbols used in the paper have their usual meaning.
- (4) Question 1 is compulsory and figures to the right indicate full marks of the question.

Q. 1. Answer the following questions in short: (10)

1. Define differential and summing amplifier.
2. An ideal operational amplifier has infinite bandwidth. (True/False)
3. Another name for a unity gain amplifier is _____.
4. In negative feedback amplifier stand for ICIS and VCIS.
5. In which multi-vibrator timer-555 the pulse width equation is $W = 1.1RC$.
6. What is Schmitt trigger and TTL clock?
7. In Hartley oscillator feedback fraction equation _____ and minimum voltage gain equation _____.
8. Define 555-timer.
9. What is flip flop?
10. For flip flop, which logic gate is used for designing.

- Q. 2. (A) Write any one of the following: (06)**
- (1) Define OP-AMP. Derive voltage gain equation for inverting amplifier.
 - (2) Write short note on instrumentation amplifier.
- (B) Write any one of the following: (04)**
- (1) What is slew rate? If the measured output voltage changes 0.8 V in 0.2 μ s, calculate slew rate.
 - (2) Write short note on summing amplifier circuit.
- Q. 3. (A) Write anyone of the following: (06)**
- (1) What is oscillator? Obtain an expression for the frequency of oscillation for Colpitt oscillator using transistor.
 - (2) What is multi-vibrator? Describe the operation of Astable 555-timmer.
- (B) Write any one of the following: (04)**
- (1) Write feedback fraction and minimum voltage gain equation for Colpitt oscillator. Find the frequency of oscillation of a Colpitt oscillator which uses $C_1 = 200$ PF, $C_2 = 300$ PF and $L = 30$ μ H.
 - (2) Design Wein bridge oscillator at $f_o = 965$ Hz frequency for value of capacitor is 0.05 μ F.
- Q. 4. (A) Write anyone of the following: (06)**
- (1) Write short note on TTL-clock circuit.
 - (2) Write short note on Schmitt trigger circuit.
- (B) Write anyone of the following: (04)**
- (1) In mono-stable timmer-555 supply voltage $V_{cc} = 12$ V with resistance 33 k Ω and capacitance 0.47 μ F. What is the minimum trigger voltage that produces an output pulse? What is the maximum capacitor voltage? What is the width of the output pulse?
 - (2) Draw functional block diagram of a timmer-555 Astable or free running mode.

Q. 5. (A) Write anyone of the following: (06)

- (1) Describe the operation of basic RS-flip flop using NOR gate without clock.
- (2) Design master-slave JK-flip flop with clock using universal logic gate.

(B) Write anyone of the following: (04)

- (1) Write short note on RS-flip flop using NAND gate without clock.
 - (2) Write short note on Edge trigger JK-flip flop with truth table.
-