

2411001103040001
EXAMINATION DECEMBER 2024
BACHELOR OF SCIENCE (INFORMATION TECHNOLOGY)
(MASTER OF SCIENCE (INFORMATION TECHNOLOGY) 5
YEAR INTEGRATED COURSE)(NCF-NEP)(THIRD SEMESTER)
MDC-FUNDAMENTAL OF ELECTRONICS - LEVEL 4

[Time: As Per Schedule]

[Max. Marks:50]

Instructions:

1. Fill up strictly the following details on your answer book

- a. Name of the Examination: **BACHELOR OF SCIENCE (INFORMATION TECHNOLOGY) (MASTER OF SCIENCE (INFORMATION TECHNOLOGY) 5 YEAR INTEGRATED COURSE) (NCF-NEP) (THIRD SEMESTER)**
- b. Name of the Subject: **MDC-FUNDAMENTAL OF ELECTRONICS - LEVEL 4**
- c. Subject Code No: **2411001103040001**

2. Sketch neat and labelled diagram wherever necessary.
3. Figures to the right indicate full marks of the question.
4. All questions are compulsory.

Seat No:

| | | | | | |
|--|--|--|--|--|--|
| | | | | | |
|--|--|--|--|--|--|

Student's Signature

Q.1 Answer the following questions.

10

[A] Define the following terms [Any Five]

5

- (1) "ONE WATT"
- (2) "ONE HERTZ"
- (3) "MUTUAL INDUCTANCE"
- (4) "PERMEABILITY"
- (5) "CAPACITANCE"
- (6) "CONDUCTOR"

[B] Answer following questions in short [Any Five]

5

- 1) _____ ohm is the resistance value for resistor color band "green, green, red, yellow, silver"
- 2) What is the usage of amplifier?
- 3) In semiconductor _____ valance electrons are in the valance orbit.
- 4) What is the full form of "MOSFET"?

- 5) _____ is the majority charge carrier in N-Type extrinsic semiconductor.
- 6) What is the Boolean equation of Exclusive- OR (X-OR) gate?

Q.2 Answer the following questions in detail 16

[A] Answer the following questions in detail [Any Two] 10

- 1) Write short note on Full wave rectifier.
- 2) Why NAND gate and NOR gate is called as universal gate?
- 3) Explain Common Emitter transistor configured circuit in detail.

[B] Answer the following questions in brief [Any Two] 6

- 1) What is ohm's law?
- 2) Describe Bubbled AND gate in detail.
- 3) Explain and kirchoff's voltage law with the help of necessary circuit diagram and equations.

Q.3 Answer the following questions in detail 16

[A] Answer the following questions in detail [Any Two] 10

- 1) Write short note on SR flip flop
- 2) Explain Parallel input serial output shift register with the help of necessary circuit diagram, timing diagram and example
- 3) Explain internal structure of PN junction diode and its Reverse biased characteristics.

[B] Answer the following questions in brief [Any Two] 6

- 1) Draw circuit diagram of 16 to 1 multiplexer.
- 2) Write short note on light emitting diode (LED).
- 3) Explain AND gate.

Q.4 Answer the following questions in detail 8

[A] Draw and explain Asynchronous Up-counter circuit with the help of necessary Timing diagram and Truth table. 5

OR

- [A] Write short note on Karnaugh-map(K-MAP) with the help of example **5**
- [B] Explain product of sum concept with the help of Example **3**

OR

- [B] Explain half adder concept with the help of necessary circuit diagram and Truth table. **3**
