

**1903000203020091**  
**EXAMINATION NOVEMBER 2024**  
**BACHELOR OF SCIENCE ( NON-NEP ) (THIRD SEMESTER)**  
**ELECTRONICS PAPER - III**  
**ELECTRONIC CIRCUITS AND APPLICATION**

[Time: As Per Schedule]

[Max. Marks: 50]

**Instructions:**

1. **1. Fill up strictly the following details on your answer book**
- a. Name of the Examination : **BACHELOR OF SCIENCE (NON-NEP) (THIRD SEMESTER)**
- b. Name of the Subject : **ELECTRONICS PAPER – III ELECTRONIC CIRCUITS AND APPLICATION**
- c. Subject Code No : **1903000203020091**
2. Sketch neat and labelled diagram wherever necessary.
3. Figures to the right indicate full marks of the question.
4. All questions are compulsory.

Seat No:

--	--	--	--	--	--

Student's Signature

**Q.1 Write the answer briefly**

**8**

1. What are the causes of instability of operating point?
2. Draw the approximate hybrid equivalent circuit for a transistor
3. What is the use of emitter follower?
4. Draw the diagram of fixed bias circuit

**Q.2**

A Derive the expression for operating point of the emitter bias circuit

**7**

B Design emitter bias circuit for  $I_{CQ} = 2\text{mA}$ ,  $V_{CC} = 20\text{V}$ ,  $\beta = 150$  and  $V_{CE} = 10\text{V}$

**7**

**OR**

A Explain how will you calculate h-parameters from the characteristics of transistor

**7**

B Using the approximate hybrid model of CC amplifier, prove that its voltage gain is approximately unity.

**7**

**Q.3**

A Derive the amplifier equations for,  $A_V$ ,  $A_i$  and  $R_I$  in terms of h-parameters

**7**

B Explain briefly Bias compensation techniques

**7**

**OR**

- A Derive the expression for stability factor in potential divider bias circuit 7
- B Explain the effect of emitter bypass capacitor on low frequency response. 7

- Q.4** A By drawing the schematic and ac equivalent diagram of two stage RC coupled amplifier, prove that the voltage gain in the mid frequency range is a constant. 7
- B Draw the complete frequency and phase response of R C coupled amplifier. 7

**OR**

- A Analyze qualitatively the collector to base bias circuit 7
- B In an RC coupled amplifier,  $R_c = 6.8\text{k}\Omega$ , effective load after the coupling capacitor is  $1\text{k}\Omega$ ,  $h_{ie} = 0.9\text{k}\Omega$ ,  $h_{fe} = 36$ ,  $C_{sh} = 1520\text{pF}$  &  $C_c = 1\ \mu\text{F}$ . Find the mid frequency gain and bandwidth of the amplifier. 7

\*\*\*\*\*