



RAN-2503000502061009

B.Sc. (Sem.-II) (NEP) Examination October - 2025

PH-SEC-2 Digital Electronics (TH)

Time: 1 Hour]

[Total Marks: 13

સૂચના : / Instructions

- (1) ઉપરોક્ત દર્શાવેલ વિગતો ઉત્તરવહી પર અવશ્ય લખવી.
Fill up strictly the above details on your answer book
- (2) પ્રશ્ન 1 ના બધા પેટા પ્રશ્નો 1 ગુણના છે.
Each sub question of Question 1 carry 1 mark each.
- (3) જમણી બાજુના અંક પ્રશ્નના પુરા ગુણ દર્શાવે છે.
Figures to the right indicate full marks of the question.

Seat No.:

--	--	--	--	--	--


Student's Signature

પ્ર.1. નીચેના પ્રશ્નોના ટૂંકમાં જવાબ આપો (કોઈ પણ 13)


13

- 1) ડિજિટલ સર્કિટ સામાન્ય રીતે એનાલોગ સર્કિટ કરતા વધુ વિશ્વસનીય કેમ માનવામાં આવે છે.?
 - A) ડિજિટલ સર્કિટ ઓછી શક્તિ વાપરે છે.
 - B) ડિજિટલ સર્કિટ વધુ જટિલ કામગીરી સંભાળી શકે છે.
 - C) ડિજિટલ સર્કિટમાં ફક્ત બે સ્થિતિઓ હોય છે, જે સિગ્નલ ઓળખને સરળ બનાવે છે.
 - D) ડિજિટલ સર્કિટનું ઉત્પાદન સસ્તું છે.
- 2) 'બીટ' શબ્દનો અર્થ શું છે?
 - A) બાઈનરી પૂર્ણાંક
 - B) બાઈનરી માહિતી
 - C) બાઈનરી અંક
 - D) બાઈનરી વસ્તુ
- 3) કયા લોજિક ગેટને ઈન્વર્ટર તરીકે ઓળખવામાં આવે છે?
 - A) AND
 - B) OR
 - C) NOT
 - D) XOR
- 4) કયો લોજિક ગેટ ફક્ત બંને ઈનપુટ ઊંચા હોય ત્યારે જ ઉચ્ચ આઉટપુટ (1) ઉત્પન્ન કરે છે ?
 - A) AND
 - B) OR
 - C) XOR
 - D) NOR
- 5) ત્રણ (3) ઈનપુટ AND ગેટમાં કેટલા ઈનપુટ સંયોજનો હશે ?
 - A) 4
 - B) 6
 - C) 8
 - D) 16

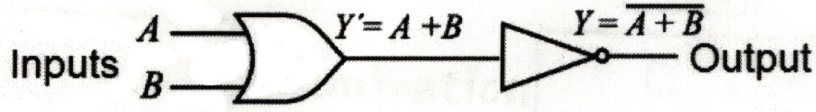- 6) ઓક્ટલ અંકો અને બાઈનરી બિટ્સ માટે સમકક્ષ કોષ્ટક દોરો.
- 7) $(110101011)_2$ ને ઓક્ટલ સંખ્યામાં રૂપાંતરિત કરો.
- 8) $(356)_{16}$ ને દશાંશ સંખ્યામાં રૂપાંતરિત કરો.
- 9) $(8E3)_{16}$ ને બાઈનરી સંખ્યામાં રૂપાંતરિત કરો.
- 10) $(489)_{10}$ ને BCD સંખ્યામાં રૂપાંતરિત કરો.
- 11) નીચે આપેલા સર્કિટ માટે ચાર અલગ અલગ ઈનપુટ સંયોજનોનું સત્યાર્થતા કોષ્ટક લખો.



- 12) આપેલા લોજિક ગેટનું નામ લખો.

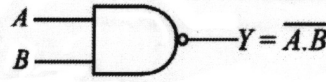


- 13) ચાર અલગ અલગ ઈનપુટ સંયોજનોનો ઉપયોગ કરીને $Y = A \cdot (\overline{A \cdot B})$ માટે સત્યાર્થતા કોષ્ટક લખો.
- 14) મૂળભૂત લોજિક ગેટ્સનાં નામ લખો.
- 15) NOR લોજિક ગેટનો લોજિક સિમ્બોલ દોરો.

ENGLISH VERSION

- Q. 1. Answer the following questions in short. (Any 13) 13**
- 1) Why are digital circuits generally considered more reliable than analogue circuits?
 - A) Digital circuits use less power
 - B) Digital circuits can handle more complex operations
 - C) Digital circuits have only two states, making signal recognition easier
 - D) Digital circuits are cheaper to produce
 - 2) What does the term 'bit' stand for?
 - A) Binary Integer
 - B) Binary Information
 - C) Binary Digit
 - D) Binary Item

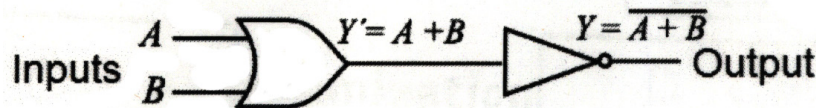- 3) Which logic gate is known as an inverter?
 - A) AND
 - B) OR
 - C) NOT
 - D) XOR
- 4) Which logic gate produces a high output (1) only when both inputs are high?
 - A) AND
 - B) OR
 - C) XOR
 - D) NOR
- 5) How many input combinations would a 3-input AND gate have?
 - A) 4
 - B) 6
 - C) 8
 - D) 16
- 6) Draw the equivalent table for octal digits and binary bits.
- 7) Convert binary number $(110101011)_2$ to octal number.
- 8) Convert Hexadecimal number $(356)_{16}$ to decimal number.
- 9) Convert Hexadecimal number $(8E3)_{16}$ to binary number.
- 10) Convert decimal number $(489)_{10}$ to BCD number
- 11) Write down the truth table of four different inputs combinations for below given circuit.



- 12) Write down the name of given logic gate.

Inputs A and B enter a NAND gate. The output of the NAND gate is labeled $Y = \overline{A.B}$.
- 13) Draw the truth table for $Y = \overline{A.(A.B)}$ using four different inputs combinations.
- 14) Write down the name of basic logic gates.
- 15) Draw the symbol of NOR gate.
