

**RAN-2411001103040001**
**B. Sc. (I.T.) NEP (Sem. - III) Examination February - 2026**
**Fundamental of Electronics**
**Time: 2 Hours ]**
**[ Total Marks: 50**
**સૂચના : / Instructions**

- (1) ઉપરોક્ત દશવિધ વિગતો ઉત્તરવહી પર અવશ્ય લખવી.  
Fill up strictly the above details on your answer book

Seat No.:

|                      |                      |                      |                      |                      |                      |
|----------------------|----------------------|----------------------|----------------------|----------------------|----------------------|
| <input type="text"/> | <input type="text"/> | <input type="text"/> | <input type="text"/> | <input type="text"/> | <input type="text"/> |
|----------------------|----------------------|----------------------|----------------------|----------------------|----------------------|

Student's Signature

**Q. 1 Answer the following questions.**
**[10]**
**Q. 1 [A] Define the following terms [Any Five]**
**[5]**

- 1) "Resistance"
- 2) "permeability"
- 3) "current"
- 4) "one Hertz (Hz)"
- 5) "one Volt"
- 6) "amplifier"

**Q. 1 [B] Answer following questions in short [Any Five]**
**[5]**

- 1) What color represents 15700 ohm resistance value of resistor?
- 2) What is the usage of Oscillator?
- 3) What is the difference between N-channel and P-channel MOSFETs?
- 4) What happens to current flow when a diode is reverse-biased?
- 5) What is the Boolean equation of NAND gate?
- 6) How is a Light Emitting Diode (LED) different from a normal diode?

**Q. 2 Answer the following questions in detail**
**(16)**
**Q. 2 [A] Answer the following questions in detail [Any Two]**
**[10]**

- 1) Write short note on Field Effect Transistor (FET).
- 2) What is the difference between a multiplexer and a demultiplexer? Explain demultiplexer with the help of necessary circuit diagram and truth table
- 3) Explain Demorgan's first and second theorem with example.

**Q. 2 [B] Answer the following questions in brief [Any Two]**
**[6]**

- 1) Describe OR gate in detail.
- 2) What is ohm's law?
- 3) Draw parallel input serial output shift register circuit diagram.

**Q. 3 Answer the following questions in detail (16)**

**Q. 3 [A] Answer the following questions in detail [Any Two] [10]**

- 1) Explain Parallel connection of resistor concept in detail with necessary circuit diagram and equations.
- 2) Explain Full wave rectifier circuit diagram and waveform in detail.
- 3) What is universal gate? Explain why NAND gate is considered as universal?

**Q. 3 [B] Answer the following questions in brief [Any Two] (06)**

- 1) Draw circuit diagram of decimal to BCD encoder.
- 2) Explain bubbled AND gate.
- 3) Write short note on voltage regulator.

**Q. 4 Answer the following questions in detail (08)**

**Q. 4 [A] Draw and explain mod-8 up counter circuit with the help of necessary Timing diagram and Truth table. [5]**

**OR**

**Q. 4 [A] Write short note on Full Adder. [5]**

**Q. 4 [B] What is magnetic flux density? How does it differ from magnetic flux? [3]**

**OR**

**Q. 4 [B] Describe Sum of product method and Product of sum method concept using given truth table. [3]**

| Input |   |   | Output |
|-------|---|---|--------|
| A     | B | C | Y      |
| 0     | 0 | 0 | 1      |
| 0     | 0 | 1 | 0      |
| 0     | 1 | 0 | 0      |
| 0     | 1 | 1 | 1      |
| 1     | 0 | 0 | 1      |
| 1     | 0 | 1 | 1      |
| 1     | 1 | 0 | 0      |
| 1     | 1 | 1 | 1      |